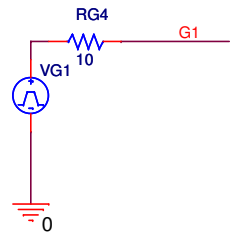


V1 = 0
V2 = 10V
TD = 2us
TR = 1ns
TF = 1ns
PW = 1us
PER = 4us



Copy and paste the GND_0 circle in order to connect the Analog GND to the appropriate wires in your circuit.

Title		
<Title>		
Size	Document Number	Rev
A4	<Doc>	<RevCode>
Date:	Tuesday, October 27, 2009	Sheet 1 of 1