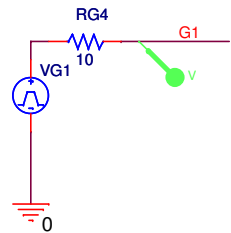


V1 = 0  
 V2 = 10V  
 TD = 2us  
 TR = 1ns  
 TF = 1ns  
 PW = 3us  
 PER = 4us



Copy and paste the GND\_0 circle in order to connect the Analog GND to the appropriate wires in your circuit.

Title		
<Title>		
Size	Document Number	Rev
A4	<Doc>	<RevCode>
Date:	Wednesday, October 28, 2009	Sheet 1 of 1